

[Dashboard](#)

[and Circuits \(iii\)](#)

Co

i  
/ 0

00 out of 100.00

ent Work!

are a highly motivated student, who takes full responsibility for your learning. A reflective learner, who recognises  
s for development and is committed to personal improvement. An organised learner who always completes class  
k and homework to a very high standard.

Question 1

Correct

Mark 2.00 out of 2.00

How many transistors would be needed to implement the following Boolean expression:

$A'B + (B + C)'$

- ☐ a. 8
- ☒ b. 9 ✓
- ☐ c. 6
- ☐ d. 10

Your answer is correct.

The correct answer is:  
9

Response history

Step	Time	Action	State	Marks
<a href="#">1</a>	17/05/22, 20:03	Started	Not yet answered	
<a href="#">2</a>	17/05/22, 20:05	Saved: 9	Answer saved	
<b>3</b>	<b>17/05/22, 22:08</b>	<b>Attempt finished</b>	<b>Correct</b>	<b>2.00</b>

Question **2**

Correct

Mark 1.00 out of 1.00

In DeMorgan's Law  $(A+B)' = A' \cdot B'$

$(A' = \text{NOT } A, B' = \text{NOT } B)$

Accordingly, which of the statement is another example to **DeMorgan's law**?

- ☐ a.  $A \cdot A' = 0$
- ☐ b.  $A \cdot B = B \cdot A$
- ☒ c.  $(AB)' = A' + B'$  ✓
- ☐ d.
- $A + A' = A$
- $A + A' = A$

Your answer is correct.

The correct answer is:

$(AB)' = A' + B'$

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:06	Saved: $(AB)' = A' + B'$	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	1.00

Question 3

Correct

Mark 1.00 out of 1.00

Simplification of the Boolean expression  $(A + B)'(C + D + E)' + (A + B)'$  :

- ☐ a.  $C + D + E$
- ☒ b.  $A'B'$  ✓
- ☐ c.  $C'D'E'$
- ☐ d.  $A'B'C'D'E'$
- ☐ e.  $A + B$

Your answer is correct.

The correct answer is:

 $A'B'$ 

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:09	Saved: $A'B'$	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	1.00

Question 4

Correct

Mark 1.00 out of 1.00

Select answers that are true

ABC=

- ☒  $(A+A').(ABC)$  ✓
- ☒  $A'A+(ABC)$  ✓
- ☒  $B(AC)$  ✓
- ☐  $B+(AC)$

Your answer is correct.

The correct answers are:

 $B(AC)$ , $A'A+(ABC)$ , $(A+A').(ABC)$ 

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:09	Saved: $(A+A').(ABC)$ ; $A'A+(ABC)$ ; $B(AC)$	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	1.00

Question **5**

Correct

Mark 1.00 out of 1.00

An equivalent representation for the Boolean expression  $A' + 1$  is:

1=TRUE 0=FALSE

- ☐ a. A
- ☒ b. 1 ✓
- ☐ c. 0
- ☐ d. A'

Your answer is correct.

The correct answer is:


1

### Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:10	Saved: 1	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	1.00

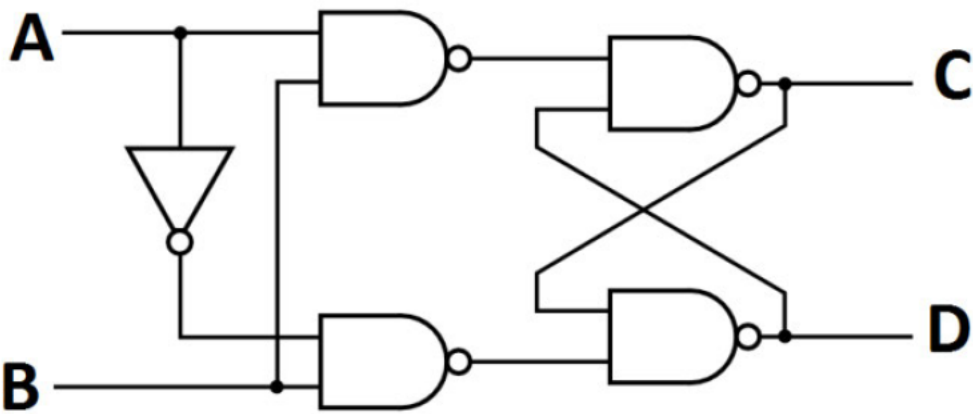Question 6  
Correct  
Mark 2.00 out of 2.00

Consider the following sequential circuit in order to answer the two following questions.



What is the output of the above flip-flop if A = 0 and B = 1?

- ☒ a. C = 0 and D = 1 ✓
- ☐ b. Pending values, not possible to calculate.
- ☐ c. C = 1 and D = 0
- ☐ d. C = 0 and D = 0
- ☐ e. C = 1 and D = 1

Your answer is correct.

The correct answer is:  
C = 0 and D = 1

Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:16	Saved: C = 0 and D = 1	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

Question 7

Correct

Mark 2.00 out of 2.00

Now suppose the input is changed to  $A = 0$  and  $B = 0$ . Preserving the current state of the flip-flop after the previous input. What is the output of the above flip-flop using the changed input?

- ☐ a. Pending values, not possible to calculate.
- ☒ b.  $C = 0$  and  $D = 1$  ✓
- ☐ c.  $C = 1$  and  $D = 0$
- ☐ d.  $C = 0$  and  $D = 0$
- ☐ e.  $C = 1$  and  $D = 1$

Your answer is correct.

The correct answer is:

$C = 0$  and  $D = 1$

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:19	Saved: $C = 0$ and $D = 1$	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

Question 8

Correct

Mark 2.00 out of 2.00

Given a full subtractor with inputs X and Y, what is X "minus" Y, given that  $X = 1$ ,  $Y = 0$  and  $Y_{out} = 1$  ?

- ☒ a. 0 ✓
- ☐ b. 2
- ☐ c. 1

Your answer is correct.

The correct answer is:

0

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:21	Saved: 0	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00



Question 9

Correct

Mark 2.00 out of 2.00

How many transistors are needed to implement the following expression?

$$A'B + A(B' + A')$$

- ☐ a. 11
- ☒ b. 15 ✓
- ☐ c. 10
- ☐ d. 5
- ☐ e. 12

Your answer is correct.

The correct answer is:  
15

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:28	Saved: 15	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

Question **10**

Correct

Mark 1.00 out of 1.00

 $A=1$  $B=0$  $C=0$  $(A.B.C+A.(B'+C'))' =$ 

Answer:



The correct answer is: 0

## Response history

Step	Time	Action	State	Marks
<a href="#">1</a>	17/05/22, 20:03	Started	Not yet answered	
<a href="#">2</a>	17/05/22, 20:30	Saved: 0	Answer saved	
<b>3</b>	<b>17/05/22, 22:08</b>	<b>Attempt finished</b>	<b>Correct</b>	<b>1.00</b>

Question **11**

Correct

Mark 1.00 out of 1.00

A=0

B=1

C=1

$(A.B.C+A.(B'+C'))' =$

Answer:

1



The correct answer is: 1

Response history


Step	Time	Action	State	Marks
<a href="#">1</a>	17/05/22, 20:03	Started	Not yet answered	
<a href="#">2</a>	17/05/22, 20:30	Saved: 1	Answer saved	
<b>3</b>	<b>17/05/22, 22:08</b>	<b>Attempt finished</b>	<b>Correct</b>	<b>1.00</b>

Question **12**

Correct

Mark 2.00 out of 2.00

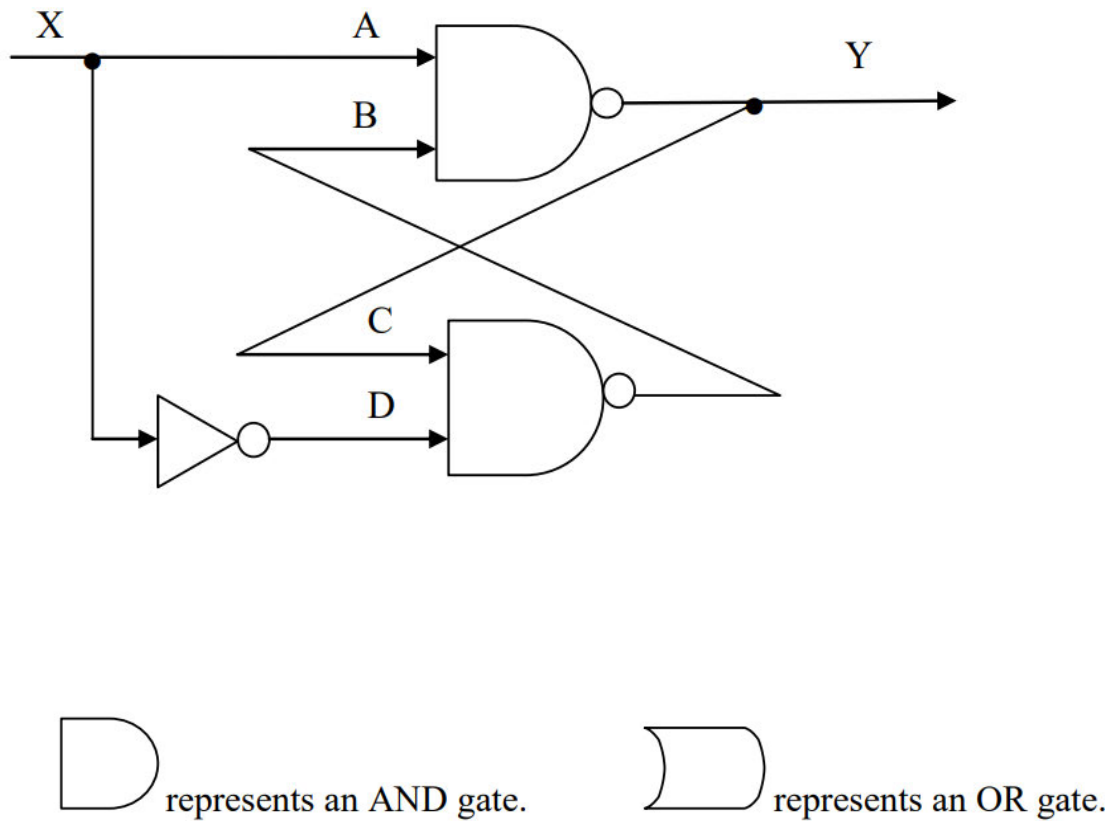Consider the flip-flop type circuit shown below. Suppose the input X is a 0. What values will A, B, C, D have? What will be the output Y?



Answer must be in the format: "answer\_A, answer\_B, answer\_C, answer\_D and answer\_Y"  
(NB: include "and" when answering this question)

Answer: 0, 0, 1, 1, and 1

✖

The correct answer is: 0,0,1,1 and 1

Comment:

Response history				
Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	

Step	Time	Action	State	Marks
2	17/05/22, 20:34	Saved: 0, 0, 1, 1, and 1	Answer saved	
3	17/05/22, 22:08	Attempt finished	Incorrect	0.00
4	25/05/22, 16:23	Manually graded 2 with comment: <a href="#">Aaqib Khan</a>	Correct	2.00

Question 13

Correct

Mark 1.00 out of 1.00

In order for an S-R Latch to work effectively (i.e., not go into a forbidden state), the outputs must always be complements.

Select one:

☒ True ✓

☐ False

The correct answer is 'True'.

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 21:32	Saved: True	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	1.00

Question **14**

Complete

Not graded

There was an error with this question so it will no longer count for marks.

Select one:

☒ True☐ False

The correct answer is 'True'.

#### Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:34	Saved: True	Answer saved	
3	17/05/22, 22:08	Attempt finished	Complete	0.00

Question **15**

Correct

Mark 2.00 out of 2.00

What is the difference between the full adders 'sum' and the full subtractors 'difference' in terms of how they are processed in our circuit:

- ☐ a. The 'sum' can be derived as being not the 'difference'.
- ☐ b. The 'difference' uses an additional not gate.
- ☐ c. They both don't use XOR gates.
- ☒ d. There is no difference. ✓

Your answer is correct.

The correct answer is:

There is no difference.

#### Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:40	Saved: There is no difference.	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

Question **16**

Correct

Mark 2.00 out of 2.00

We currently have a number of joint full adders that let us add 3 digit binary numbers. How many more transistors would we be required to add to our circuit in order to transform it into a full subtractor?

Answer:  

The correct answer is: 6

## Response history

Step	Time	Action	State	Marks
<a href="#">1</a>	17/05/22, 20:03	Started	Not yet answered	
<a href="#">2</a>	17/05/22, 21:47	Saved: 6	Answer saved	
<b>3</b>	<b>17/05/22, 22:08</b>	<b>Attempt finished</b>	<b>Correct</b>	<b>2.00</b>



Question **17**

Correct

Mark 2.00 out of 2.00

We have constructed a half subtractor, when working in base 10, if borrowing is necessary, how many units will be required to be borrowed?

- ☒ a. 10 ✓
- ☐ b. 2
- ☐ c. 1
- ☐ d. Can't know beforehand.

Your answer is correct.

The correct answer is:  
10

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:41	Saved: 10	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

Question **18**

Correct

Mark 3.00 out of 3.00

Complete the following full subtractor truth table.

Inputs			Outputs	
A	B	Borrow <sub>in</sub>	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	<b>a</b>	0	1	1
0	1	1	0	<b>c</b>
1	0	0	1	0
1	0	1	<b>b</b>	0
1	1	0	0	0
1	1	1	1	1

- ☒ a. a = 1, b = 0, c = 1 ✓
- ☐ b. a = 1, b = 1, c = 1
- ☐ c. a = 0, b = 1, c = 0
- ☐ d. a = 1, b = 0, c = 0

Your answer is correct.

The correct answer is:

a = 1, b = 0, c = 1

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:50	Saved: a = 1, b = 0, c = 1	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	3.00

Question **19**

Correct

Mark 2.00 out of 2.00

Considering the full subtractor discussed in class (A-B, with B<sub>in</sub> and B<sub>out</sub>) we can say that B<sub>in</sub> will only be 1 if  $A \leq B + B_{out}$ .

Select one:

☐ True☒ False ✓

The correct answer is 'False'.

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:53	Saved: False	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00


Question **20**

Correct

Mark 2.00 out of 2.00

Given the Diagram below determine the values of X and Y given :

S = 0, R = 1

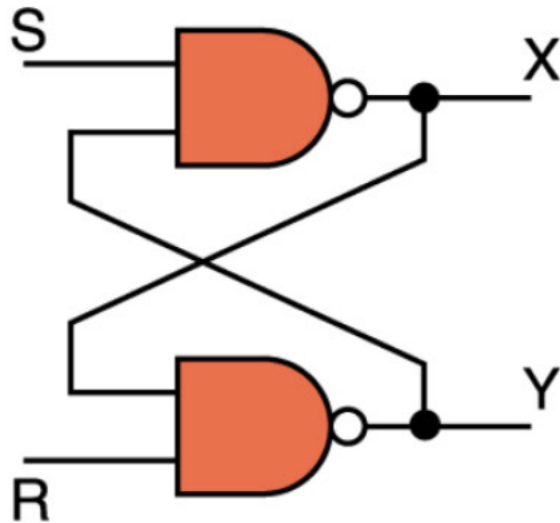

Select one:

- ☒ a. X=1, Y=0. ✓
- ☐ b. The circuit oscillates between 0s and 1s.
- ☐ c. X=0, Y=0.
- ☐ d. X=0, Y=1.
- ☐ e. X=1, Y=1.

The correct answer is: X=1, Y=0.

### Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:54	Saved: X=1, Y=0.	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

Question **21**

Correct

Mark 1.00 out of 1.00

Which is the correct logic gate used to implement an S-R latch?

- ☐ a. 2 NOR gates.
- ☐ b. 2 NAND gates.
- ☒ c. Any of the above. ✓

Your answer is correct.

The correct answer is:

Any of the above.

#### Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 20:55	Saved: Any of the above.	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	1.00

Question **22**

Correct

Mark 2.00 out of 2.00

We have a SR latch (constructed using NAND gates) that is in a forbidden state, this tells us that:

- ☐ a.  $S=1$  and  $R=0$
- ☐ b.  $S=1$  and  $R=1$
- ☐ c.  $S=0$  and  $R=1$
- ☒ d.  $S=0$  and  $R=0$  ✓

Your answer is correct.

The correct answer is:

$S=0$  and  $R=0$

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 21:01	Saved: $S=0$ and $R=0$	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

Question **23**

Complete

Not graded

1. When both inputs to an S-R latch constructed with 2 NOR gates is 1 we call it the forbidden state. Why is this state not used? (This is a select all that are correct type question)

- a. The output of the latch become unpredictable.
- b. The latch flips the 2 inputs, creating an unreliable way of storing bits.
- c. The latch does not flip the 2 inputs, creating an unreliable way of storing bits.
- d. The first property of the latch is violated as both outputs are 0.

- ☐ i. a) and d).
- ☐ ii. a), c) and d).
- ☐ iii. b) and d).
- ☒ iv. None of the above.

Your answer is incorrect.

The correct answer is:

a) and d).

### Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 21:08	Saved: a) and d).	Answer saved	
3	17/05/22, 21:27	Saved: None of the above.	Answer saved	
4	17/05/22, 22:08	Attempt finished	Complete	0.00


Question 24

Correct

Mark 1.00 out of 1.00

Given the Diagram below determine the values of X and Y given :

$S = 1, R = 0$

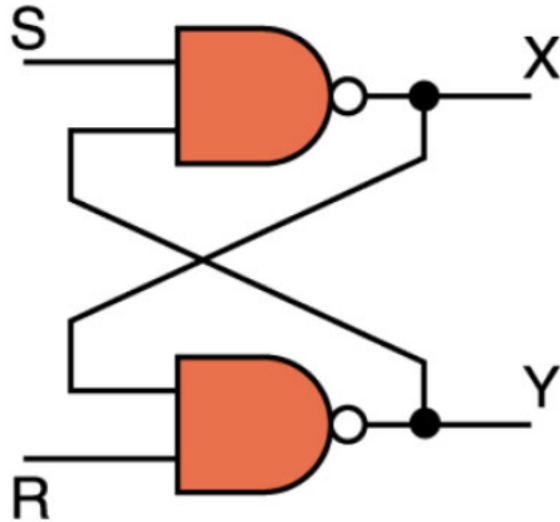

Select one:

- ☐ a.  $X = 0, Y = 0$
- ☐ b.  $X = 1, Y = 0$
- ☐ c.  $X = 1, Y = 1$
- ☒ d.  $X = 0, Y = 1$  ✓
- ☐ e. The circuit oscillates between 0s and 1s.

The correct answer is:  $X = 0, Y = 1$

#### Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 21:09	Saved: $X = 0, Y = 1$	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	1.00



Question **25**

Correct

Mark 2.00 out of 2.00

How many bits can a S-R latch store?

- ☒ a. 1 ✓
- ☐ b. 2
- ☐ c. 8
- ☐ d. None of the above.

Your answer is correct.

The correct answer is:

1

## Response history

Step	Time	Action	State	Marks
<a href="#">1</a>	17/05/22, 20:03	Started	Not yet answered	
<a href="#">2</a>	17/05/22, 21:10	Saved: 1	Answer saved	
<b>3</b>	<b>17/05/22, 22:08</b>	<b>Attempt finished</b>	<b>Correct</b>	<b>2.00</b>


Question **26**

Correct

Mark 2.00 out of 2.00

Given the Diagram below determine the values of X and Y given :

S = 1, R = 0

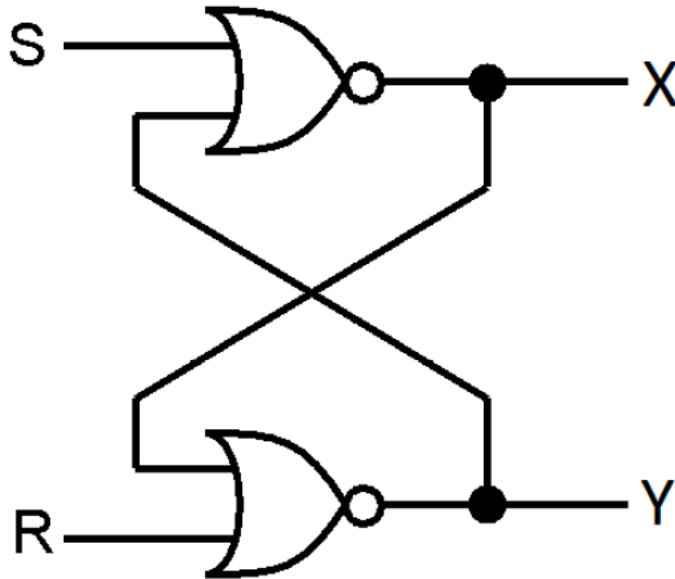

Select one:

- ☐ a. The circuit oscillates between 0s and 1s.
- ☐ b. X=0, Y=0.
- ☐ c. X=1, Y=1.
- ☐ d. X=1, Y=0.
- ☒ e. X=0, Y=1. ✓

The correct answer is: X=0, Y=1.

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 21:16	Saved: X=0, Y=1.	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

Question **27**

Complete

Not graded

We have a S-R latch storing the value 0, if R is momentarily changed to 0 what happens to our stored value in the circuit?

- ☐ a. It becomes 1.
- ☐ b. It fluctuates infinitely between 1 and 0.
- ☒ c. It remains 0.
- ☐ d. None of the above.

Your answer is incorrect.

The correct answer is:  
It becomes 1.

## Response history


Step	Time	Action	State	Marks
<a href="#">1</a>	17/05/22, 20:03	Started	Not yet answered	
<a href="#">2</a>	17/05/22, 21:18	Saved: It remains 0.	Answer saved	
<b>3</b>	<b>17/05/22, 22:08</b>	<b>Attempt finished</b>	<b>Complete</b>	<b>0.00</b>

Question 28

Correct

Mark 2.00 out of 2.00

Consider the latch below;

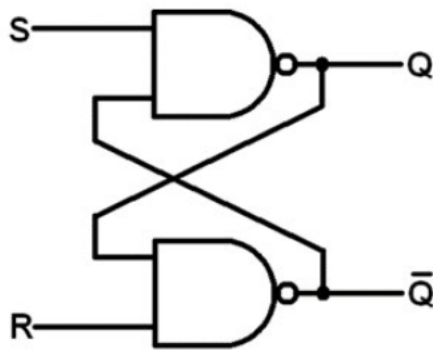

Which values of R and S will preserve the output of the previous state of the latch?

- ☐ a. R=1, S=0
- ☐ b. R=0, S=0
- ☒ c. R=1, S=1 ✓
- ☐ d. None of the above.

Your answer is correct.

The correct answer is:

R=1, S=1

## Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 21:21	Saved: R=1, S=1	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

Question **29**

Correct

Mark 2.00 out of 2.00

We have a memory device that uses 2000 SR latches to store data on, how many bytes of memory can the device store?

Answer:

✓

The correct answer is: 250

Response history

Step	Time	Action	State	Marks
<a href="#">1</a>	17/05/22, 20:03	Started	Not yet answered	
<a href="#">2</a>	17/05/22, 21:21	Saved: 250	Answer saved	
<b>3</b>	<b>17/05/22, 22:08</b>	<b>Attempt finished</b>	<b>Correct</b>	<b>2.00</b>


Question 30

Correct

Mark 2.00 out of 2.00

Given the Diagram below determine the values of X and Y given :

S = 1, R = 1

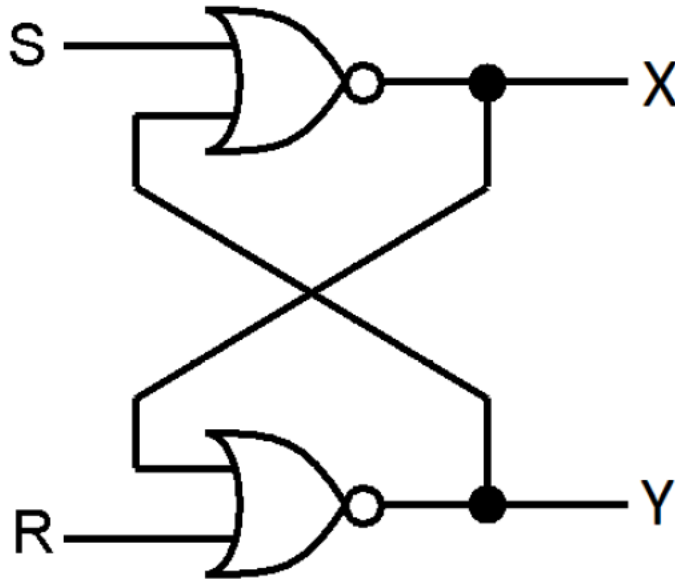

Select one:

- ☐ a. X=1, Y=0
- ☐ b. The circuit oscillates between 0s and 1s.
- ☐ c. X=1, Y=1
- ☐ d. X=0, Y=1
- ☒ e. X=0, Y=0. ✓

The correct answer is: X=0, Y=0.

### Response history

Step	Time	Action	State	Marks
1	17/05/22, 20:03	Started	Not yet answered	
2	17/05/22, 21:23	Saved: X=0, Y=0.	Answer saved	
3	17/05/22, 22:08	Attempt finished	Correct	2.00

◀ Lesson 3- Gates and Circuits by Dr. Ritesh Ajoodha

Jump to...

[DNF \(Zero-Rated Download\) \(Additional material by Mr. Brandon Ingram\)](#) ►